

WEEK: 15

Week Beginning: 29-6-20

Subject: SCIENCE

Year: 9

Lesson Objective:

- Go over homework
- Circuit and resistance practical
- Electricity in the home

Keywords/ Concepts

- Current, resistance, home

Class Worksheets

- Questions below

Homework

- Notes

Additional Notes


- Attach all the classroom worksheets and homework worksheets to this lesson plan and email together.
- Assume the students don't have revision guides and workbooks. Attach all the pages you want them to have.

Parallel Circuits

Parallel circuits can be a little bit trickier to wrap your head around, but they're much more useful than series circuits. Most electronics use a combination of series and parallel circuitry.

Parallel Circuits — Independence and Isolation

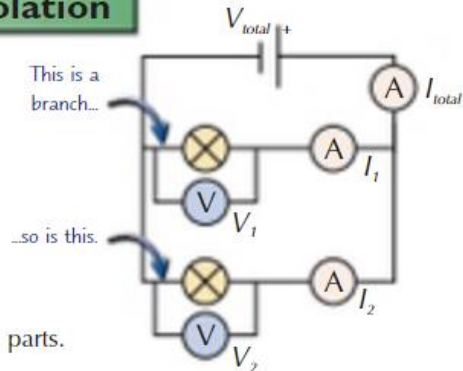- 1) In parallel circuits, each component is separately connected to the +ve and -ve of the supply (except ammeters, which are always connected in series).
- 2) If you remove or disconnect one of them, it will hardly affect the others at all.
- 3) This is obviously how most things must be connected, for example in cars and in household electrics. You have to be able to switch everything on and off separately.
- 4) Everyday circuits often include a mixture of series and parallel parts.



Potential Difference is the Same Across All Components

- 1) In parallel circuits all components get the full source pd, so the voltage is the same across all components: $V_1 = V_2 = V_3 = \dots$
- 2) This means that identical bulbs connected in parallel will all be at the same brightness.

Current is Shared Between Branches

- 1) In parallel circuits the total current flowing around the circuit is equal to the total of all the currents through the separate components: $I_{total} = I_1 + I_2 + \dots$
- 2) In a parallel circuit, there are junctions where the current either splits or rejoins. The total current going into a junction has to equal the total current leaving it.
- 3) If two identical components are connected in parallel then the same current will flow through each component.

Adding a Resistor in Parallel Reduces the Total Resistance

- 1) If you have two resistors in parallel, their total resistance is less than the resistance of the smallest of the two resistors.
- 2) This can be tough to get your head around, but think about it like this:
 - In parallel, both resistors have the same potential difference across them as the source.
 - This means the 'pushing force' making the current flow is the same as the source potential difference for each resistor that you add.
 - But by adding another loop, the current has more than one direction to go in.
 - This increases the total current that can flow around the circuit. Using $V = IR$, an increase in current means a decrease in the total resistance of the circuit.


Classwork

1. Which has higher resistance, two resistors in a series circuit or the two same resistors in a parallel circuit?

1 **Figure 1** shows a series circuit.

4-6

Figure 1

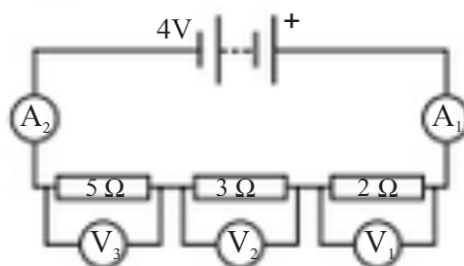

1.1 Calculate the total resistance in the circuit.

[2 marks]

1.2 The current through A_1 is 0.4 A.
What is the current through A_2 ? Explain your answer.

[2 marks]

1.3 V_1 reads 0.8 V and V_2 reads 1.2 V.
Calculate the reading on V_3 .

[2 marks]

2 A parallel circuit is connected as shown in **Figure 2**.

7-9

Figure 2

2.1 Give the reading on voltmeter V_1 .


[1 mark]

2.2 Calculate the reading on ammeter A_1 .

[3 marks]

2.3 Calculate the reading on ammeter A_2 .

[2 marks]

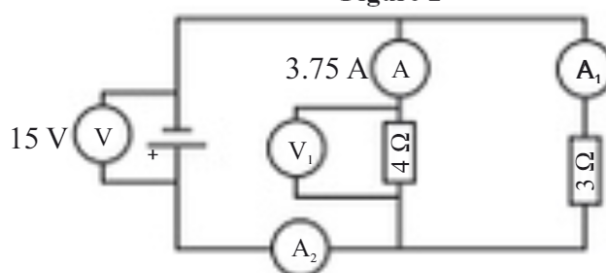

Power of Electrical Appliances

You can think about **electrical circuits** in terms of **energy transfer** — the charge carriers take energy around the circuit. When they go through an electrical component energy is transferred to make the component work.

Energy is Transferred from Cells and Other Sources

- 1) You know from page 17 that a moving charge **transfers energy**. This is because the charge **does work against** the **resistance** of the circuit. (Work done is the **same** as energy transferred, p.18.)
- 2) Electrical appliances are designed to **transfer energy** to components in the circuit when a **current** flows.

Kettles transfer energy **electrically** from the mains ac supply to the **thermal** energy store of the heating element inside the kettle.



Energy is transferred **electrically** from the **battery** of a handheld fan to the **kinetic** energy store of the fan's motor.



- 3) Of course, **no** appliance transfers **all** energy completely usefully. The **higher** the **current**, the more energy is transferred to the **thermal** energy stores of the components (and then the surroundings). You can calculate the **efficiency** of any electrical appliance — see p.28.

Energy Transferred Depends on the Power

- 1) The **total** energy transferred by an appliance depends on **how long** the appliance is on for and its **power**.
- 2) The **power** of an appliance is the energy that it **transfers per second**. So the **more** energy it transfers in a given time, the **higher** its power.
- 3) The amount of **energy transferred by electrical work** is given by:

$$\text{Energy transferred (J)} = \text{Power (W)} \times \text{Time (s)}$$

$$E = Pt$$

This equation should be familiar from page 23.

EXAMPLE:

A 600 W microwave is used for 5 minutes. How long (in minutes) would a 750 W microwave take to do the same amount of work?

- 1) Calculate the **energy transferred** by the **600 W** microwave in **five minutes**.
- 2) **Rearrange** $E = Pt$ and **sub in** the **energy** you calculated and the **power** of the 750 W microwave.
- 3) **Convert** the time back to **minutes**.

$$E = Pt = 600 \times (5 \times 60) = 180\,000 \text{ J}$$

$$t = E \div P = 180\,000 \div 750 = 240 \text{ s}$$

$$240 \div 60 = 4 \text{ minutes}$$

So the 750 W microwave would take 4 minutes to do the same amount of work.

Remember that the time must be in seconds.

- 4) Appliances are often given a **power rating** — they're labelled with the **maximum** safe power that they can operate at. You can usually take this to be their **maximum operating power**.
- 5) The power rating tells you the **maximum** amount of **energy** transferred between stores **per second** when the appliance is in use.
- 6) This helps customers choose between models — the **lower** the power rating, the **less** electricity an appliance uses in a given time and so the **cheaper** it is to run.
- 7) But a higher power **doesn't** necessarily mean that it transfers **more** energy **usefully**. An appliance may be **more powerful** than another, **but less efficient**, meaning that it might still only transfer the **same amount** of energy (or even **less**) to useful stores (see p.28).

More on Power


As you've seen, the **power** of a device tells you how much **energy** it transfers **per second**. In electrical systems, there are a load of useful formulas you can use to calculate energy and power.

Potential Difference is Energy Transferred per Charge Passed

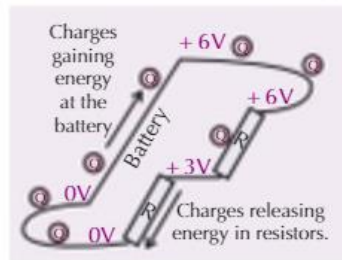- 1) When an electrical **charge** goes through a **change** in potential difference, **energy** is **transferred**.
- 2) Energy is **supplied** to the charge at the **power source** to 'raise' it through a potential.
- 3) The charge **gives up** this energy when it '**falls**' through any **potential drop** in **components** elsewhere in the circuit.
- 4) The formula is really simple:

$$E = QV$$

Energy transferred (J)
Potential difference (V)



- 5) That means that a battery with a **bigger pd** will supply **more energy** to the circuit for every **coulomb** of charge which flows round it, because the charge is raised up "**higher**" at the start.

EXAMPLE:

The motor in an electric toothbrush is attached to a 3 V battery. 140 C of charge passes through the circuit as it is used. Calculate the energy transferred.

$$E = QV = 140 \times 3 = 420 \text{ J}$$

This energy is transferred to the kinetic energy store of the motor, as well as to the thermal energy stores of the surroundings.

Power Also Depends on Current and Potential Difference

- 1) As well as energy transferred in a given time, the **power** of an appliance can be found with:

$$\text{Power (W)} = \text{Potential difference (V)} \times \text{Current (A)}$$

$$P = VI$$

EXAMPLE:

A 1.0 kW hair dryer is connected to a 230 V supply. Calculate the current through the hair dryer. Give your answer to two significant figures.

- | | |
|---|---|
| 1) Rearrange the equation for current. | $I = P \div V$ |
| 2) Make sure your units are correct. | $1.0 \text{ kW} = 1000 \text{ W}$ |
| 3) Then just stick in the numbers that you have. | $I = 1000 \div 230 = 4.34... = 4.3 \text{ A (to 2 s.f.)}$ |

- 2) You can also find the power if you **don't know** the **potential difference**. To do this, stick $V = IR$ from page 41 into $P = VI$, which gives you:

$$P = I^2R$$

Resistance (Ω)